

## Physics II Exam 2 Review

Christopher Lane<sup>1,2</sup> Justin Lucas<sup>1,3</sup> Julia Bielaski<sup>1,2</sup>

<sup>1</sup>Department Physics, Clarkson University

<sup>2</sup>Department Mathematics, Clarkson University

<sup>3</sup>Department Electrical and Computer Engineering, Clarkson University

March 1, 2011

# Outline

- 1 Must knows!!
- 2 Problems
  - Problem 1
  - Problem 2
- 3 Multiple Choice
  - Chapter 24: Electric Potential
  - Chapter 25: Capacitance
  - Chapter 26: Current and Resistance
  - Chapter 27: Circuits

## Must Knows!!

Constants:

$$k = \frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 \text{ Nm}^2/\text{C}^2$$


$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$

$$e = 1.602 \times 10^{-19} \text{ C}$$

# Problems

## Problem 1


Consider the following resistor circuit:

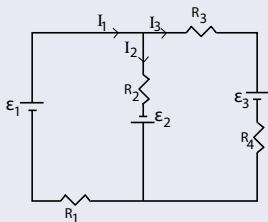

- A Find  $I_1$ ,  $I_2$ , and  $I_3$  and state if the assumed directions are correct.
- B Find the power dissipated in each resistor.
- C Find the power delivered to or by each battery.
- D Find the magnitude of potential difference between the two nodes in the circuit.
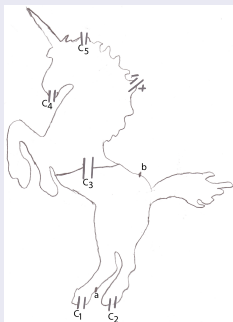
## Problem 2

Consider the following capacitor circuit:



- A Calculate the equivalent capacitance.
- B Find the charge and potential difference across each capacitor.
- C Find the potential difference between points *a* and *b*.
- D What is the total energy of this system? If the separation in  $C_5 = 10 \times 10^{-6} \text{ m}$  what is its electric field?


## Multiple Choice

## Chapter 24: Electric Potential


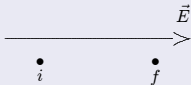
## Question 1

An electron moves from point  $i$  to point  $f$ , in the direction of a uniform electric field. During this displacement:



- A the work done by the field is positive and the potential energy of the electron-field system increases
- B the work done by the field is negative and the potential energy of the electron-field system increases
- C the work done by the field is positive and the potential energy of the electron-field system decreases
- D the work done by the field is negative and the potential energy of the electron-field system decreases
- E the work done by the field is positive and the potential energy of the electron-field system does not change

## Question 1

An electron moves from point  $i$  to point  $f$ , in the direction of a uniform electric field. During this displacement:



- A the work done by the field is positive and the potential energy of the electron-field system increases
- B the work done by the field is negative and the potential energy of the electron-field system increases
- C the work done by the field is positive and the potential energy of the electron-field system decreases
- D the work done by the field is negative and the potential energy of the electron-field system decreases
- E the work done by the field is positive and the potential energy of the electron-field system does not change

Answer: B

## Question 2

Choose the correct statement:

- A A proton tends to go from a region of low potential to a region of high potential
- B The potential of a negatively charged conductor must be negative
- C If  $\vec{E} = 0$  at a point P then  $V$  must be zero at P
- D If  $V = 0$  at a point P then  $\vec{E}$  must be zero at P
- E None of the above are correct

## Question 2


Choose the correct statement:

- A A proton tends to go from a region of low potential to a region of high potential
- B The potential of a negatively charged conductor must be negative
- C If  $\vec{E} = 0$  at a point P then V must be zero at P
- D If  $V = 0$  at a point P then  $\vec{E}$  must be zero at P
- E None of the above are correct

Answer: E
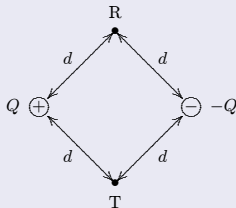
## Question 3


Points R and T are each a distance  $d$  from each of two particles with charges of equal magnitudes and opposite signs as shown. If  $k = \frac{1}{4\pi\epsilon_0}$ , the work required to move a particle with a negative charge  $q$  from R to T is:



- A 0  
B  $\frac{kqQ}{d^2}$   
C  $\frac{kqQ}{d}$   
D  $\frac{kqQ}{\sqrt{2}d}$   
E  $\frac{kqQ}{2d}$
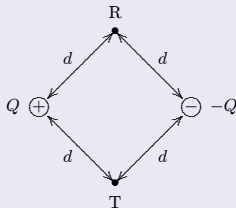
## Question 3

Points R and T are each a distance  $d$  from each of two particles with charges of equal magnitudes and opposite signs as shown. If  $k = \frac{1}{4\pi\epsilon_0}$ , the work required to move a particle with a negative charge  $q$  from R to T is:



- A 0  
B  $\frac{kqQ}{d^2}$   
C  $\frac{kqQ}{d}$   
D  $\frac{kqQ}{\sqrt{2}d}$   
E  $\frac{kqQ}{2d}$

Answer: A

### Question 4

An electron volt is:

- A the force acting on an electron in a field of  $1 \frac{N}{C}$
- B the force required to move an electron 1 meter
- C the energy gained by an electron in moving through a potential difference of 1 volt
- D the energy needed to move an electron through 1 meter in any electric field
- E the work done when 1 coulomb of charge is moved through a potential difference of 1 volt

### Question 4

An electron volt is:


- A the force acting on an electron in a field of  $1 \frac{N}{C}$
- B the force required to move an electron 1 meter
- C the energy gained by an electron in moving through a potential difference of 1 volt
- D the energy needed to move an electron through 1 meter in any electric field
- E the work done when 1 coulomb of charge is moved through a potential difference of 1 volt

Answer: C


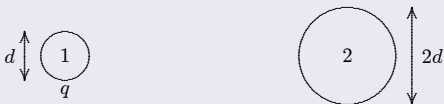
## Question 5


Two conducting spheres, one having twice the diameter of the other, are separated by a distance large compared to their diameters. The smaller sphere (1) has charge  $q$  and the larger sphere (2) is uncharged. If the spheres are then connected by a long thin wire:



- A 1 and 2 have the same potential
- B 2 has twice the potential of 1
- C 2 has half the potential of 1
- D 1 and 2 have the same charge
- E all of the charge is dissipated
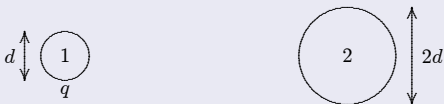
## Question 5

Two conducting spheres, one having twice the diameter of the other, are separated by a distance large compared to their diameters. The smaller sphere (1) has charge  $q$  and the larger sphere (2) is uncharged. If the spheres are then connected by a long thin wire:



- A 1 and 2 have the same potential
- B 2 has twice the potential of 1
- C 2 has half the potential of 1
- D 1 and 2 have the same charge
- E all of the charge is dissipated

Answer: A

### Question 6

A hollow metal sphere is charged to a potential  $V$ . The potential at its center is:

- A  $V$
- B  $0$
- C  $-V$
- D  $2V$
- E  $\pi V$

### Question 6

A hollow metal sphere is charged to a potential  $V$ . The potential at its center is:

- A  $V$
- B  $0$
- C  $-V$
- D  $2V$
- E  $\pi V$

Answer: A

### Question 7

In a certain region of space the electric potential increases uniformly from east to west and does not vary in any other direction. The electric field:

- A points east and varies with position
- B points east and does not vary with position
- C points west and varies with position
- D points west and does not vary with position
- E points north and does not vary with position

### Question 7

In a certain region of space the electric potential increases uniformly from east to west and does not vary in any other direction. The electric field:

- A points east and varies with position
- B points east and does not vary with position
- C points west and varies with position
- D points west and does not vary with position
- E points north and does not vary with position

Answer: B

## Chapter 25: Capacitance

### Question 1

A capacitor  $C$  has a charge  $Q$ . The actual charges on its plates are:

- A  $Q, Q$
- B  $\frac{Q}{2}, \frac{Q}{2}$
- C  $Q, -Q$
- D  $\frac{Q}{2}, -\frac{Q}{2}$
- E  $Q, 0$



### Question 1

A capacitor  $C$  has a charge  $Q$ . The actual charges on its plates are:

A  $Q, Q$

B  $\frac{Q}{2}, \frac{Q}{2}$

C  $Q, -Q$

D  $\frac{Q}{2}, -\frac{Q}{2}$

E  $Q, 0$

Answer: C

## Question 2

The capacitance of a parallel-plate capacitor is:

- A proportional to the plate area
- B proportional to the charge stored
- C independent of any material inserted between the plates
- D proportional to the potential difference of the plates
- E proportional to the plate separation

## Question 2

The capacitance of a parallel-plate capacitor is:

- A proportional to the plate area
- B proportional to the charge stored
- C independent of any material inserted between the plates
- D proportional to the potential difference of the plates
- E proportional to the plate separation

Answer: A

### Question 3

The capacitance of a parallel-plate capacitor can be increased by:

- A increasing the charge
- B decreasing the charge
- C increasing the plate separation
- D decreasing the plate separation
- E decreasing the plate area

### Question 3

The capacitance of a parallel-plate capacitor can be increased by:

- A increasing the charge
- B decreasing the charge
- C increasing the plate separation
- D decreasing the plate separation
- E decreasing the plate area

Answer: D

### Question 4

The capacitance of a cylindrical capacitor can be increased by:

- A decreasing both the radius of the inner cylinder and the length
- B increasing both the radius of the inner cylinder and the length
- C increasing the radius of the outer cylindrical shell and decreasing the length
- D decreasing the radius of the inner cylinder and increasing the radius of the outer cylindrical shell
- E only by decreasing the length

### Question 4

The capacitance of a cylindrical capacitor can be increased by:

- A decreasing both the radius of the inner cylinder and the length
- B increasing both the radius of the inner cylinder and the length
- C increasing the radius of the outer cylindrical shell and decreasing the length
- D decreasing the radius of the inner cylinder and increasing the radius of the outer cylindrical shell
- E only by decreasing the length

Answer: B

### Question 5

Let  $Q$  denote charge,  $V$  denote potential difference, and  $U$  denote stored energy. Of these quantities, capacitors in series must have the same:

- A  $Q$  only
- B  $V$  only
- C  $U$  only
- D  $Q$  and  $U$  only
- E  $V$  and  $U$  only



### Question 5

Let  $Q$  denote charge,  $V$  denote potential difference, and  $U$  denote stored energy. Of these quantities, capacitors in series must have the same:

- A  $Q$  only
- B  $V$  only
- C  $U$  only
- D  $Q$  and  $U$  only
- E  $V$  and  $U$  only

Answer: A

### Question 6

Capacitors  $C_1$  and  $C_2$  are connected in series. The equivalent capacitance is given by:

A  $\frac{C_1 C_2}{C_1 + C_2}$

B  $\frac{C_1 + C_2}{C_1 C_2}$

C  $\frac{1}{C_1 + C_2}$

D  $\frac{C_1}{C_2}$

E  $C_1 + C_2$

### Question 6

Capacitors  $C_1$  and  $C_2$  are connected in series. The equivalent capacitance is given by:

A  $\frac{C_1 C_2}{C_1 + C_2}$

B  $\frac{C_1 + C_2}{C_1 C_2}$

C  $\frac{1}{C_1 + C_2}$

D  $\frac{C_1}{C_2}$

E  $C_1 + C_2$

Answer: A

### Question 7

Two identical capacitors, each with capacitance  $C$ , are connected in parallel and the combination is connected in series to a third identical capacitor. The equivalent capacitance of this arrangement is:

- A  $\frac{2C}{3}$
- B  $C$
- C  $\frac{3C}{2}$
- D  $2C$
- E  $3C$

### Question 7

Two identical capacitors, each with capacitance  $C$ , are connected in parallel and the combination is connected in series to a third identical capacitor. The equivalent capacitance of this arrangement is:

A  $\frac{2C}{3}$

B  $C$

C  $\frac{3C}{2}$

D  $2C$

E  $3C$

Answer: A

## Chapter 26: Current and Resistance

### Question 1

A car battery is rated at  $80 \text{ A} \cdot \text{h}$ . An ampere-hour is a unit of:

- A power
- B energy
- C current
- D charge
- E force

### Question 1

A car battery is rated at  $80 \text{ A} \cdot \text{h}$ . An ampere-hour is a unit of:

- A power
- B energy
- C current
- D charge
- E force

Answer: D



## Question 2

Current is a measure of:

- A force that moves a charge past a point
- B resistance to the movement of a charge past a point
- C energy used to move a charge past a point
- D amount of charge that moves past a point per unit time
- E speed with which a charge moves past a point

## Question 2

Current is a measure of:

- A force that moves a charge past a point
- B resistance to the movement of a charge past a point
- C energy used to move a charge past a point
- D amount of charge that moves past a point per unit time
- E speed with which a charge moves past a point

Answer: D

### Question 3

Two wires made of different materials have the same uniform current density. They carry the same current only if:

- A their lengths are the same
- B their cross-sectional areas are the same
- C both their lengths and cross-sectional areas are the same
- D the potential differences across them are the same
- E the electric fields in them are the same

### Question 3

Two wires made of different materials have the same uniform current density. They carry the same current only if:

- A their lengths are the same
- B their cross-sectional areas are the same
- C both their lengths and cross-sectional areas are the same
- D the potential differences across them are the same
- E the electric fields in them are the same

Answer: B

### Question 4

If the potential difference across a resistor is doubled:

- A only the current is doubled
- B only the current is halved
- C only the resistance is doubled
- D only the resistance is halved
- E both the current and resistance are doubled

### Question 4

If the potential difference across a resistor is doubled:

- A only the current is doubled
- B only the current is halved
- C only the resistance is doubled
- D only the resistance is halved
- E both the current and resistance are doubled

Answer: A

### Question 5

Of the following, the copper conductor that has the least resistance is:

- A thin, long and hot
- B thick, short and cool
- C thick, long and hot
- D thin, short and cool
- E thin, short and hot

### Question 5

Of the following, the copper conductor that has the least resistance is:


- A thin, long and hot
- B thick, short and cool
- C thick, long and hot
- D thin, short and cool
- E thin, short and hot

Answer: B



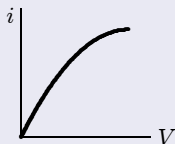
### Question 6

Which of the following graphs best represents the current-voltage relationship for a device that obeys Ohm's law?



A

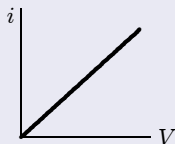


B



C




D

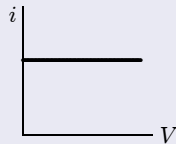


E
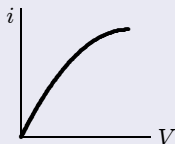
### Question 6

Which of the following graphs best represents the current-voltage relationship for a device that obeys Ohms law?



A

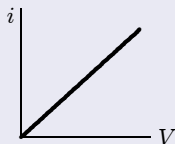


B



C



D

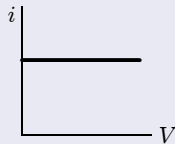

E

Answer: B

### Question 7

For a cylindrical resistor made of ohmic material, the resistance does NOT depend on:

- A the current
- B the length
- C the cross-sectional area
- D the resistivity
- E the electron drift velocity

### Question 7

For a cylindrical resistor made of ohmic material, the resistance does NOT depend on:

- A the current
- B the length
- C the cross-sectional area
- D the resistivity
- E the electron drift velocity

Answer: A

### Question 8

You wish to triple the rate of energy dissipation in a heating device. To do this you could triple:

- A the potential difference keeping the resistance the same
- B the current keeping the resistance the same
- C the resistance keeping the potential difference the same
- D the resistance keeping the current the same
- E both the potential difference and current

### Question 8

You wish to triple the rate of energy dissipation in a heating device. To do this you could triple:

- A the potential difference keeping the resistance the same
- B the current keeping the resistance the same
- C the resistance keeping the potential difference the same
- D the resistance keeping the current the same
- E both the potential difference and current

Answer: D

## Chapter 27: Circuits

### Question 1

Four wires meet at a junction. The first carries 4 A into the junction, the second carries 5 A out of the junction, and the third carries 2 A out of the junction. The fourth carries:

- A 7 A out of the junction
- B 7 A into the junction
- C 3 A out of the junction
- D 3 A into the junction
- E 1 A into the junction



### Question 1

Four wires meet at a junction. The first carries 4 A into the junction, the second carries 5 A out of the junction, and the third carries 2 A out of the junction. The fourth carries:

- A 7 A out of the junction
- B 7 A into the junction
- C 3 A out of the junction
- D 3 A into the junction
- E 1 A into the junction

Answer: D

## Question 2

In the context of the loop and junctions rules for electrical circuits a junction is:

- A where a wire is connected to a resistor
- B where a wire is connected to a battery
- C where only two wires are joined
- D where three or more wires are joined
- E where a wire is bent

## Question 2

In the context of the loop and junctions rules for electrical circuits a junction is:

- A where a wire is connected to a resistor
- B where a wire is connected to a battery
- C where only two wires are joined
- D where three or more wires are joined
- E where a wire is bent

Answer: D

### Question 3

By using only two resistors,  $R_1$  and  $R_2$ , a student is able to obtain resistances of  $3\ \Omega$ ,  $4\ \Omega$ ,  $12\ \Omega$ , and  $16\ \Omega$ . The values of  $R_1$  and  $R_2$  (in ohms) are:

- A 3, 4
- B 2, 12
- C 3, 16
- D 4, 12
- E 4, 16

### Question 3

By using only two resistors,  $R_1$  and  $R_2$ , a student is able to obtain resistances of  $3 \Omega$ ,  $4 \Omega$ ,  $12 \Omega$ , and  $16 \Omega$ . The values of  $R_1$  and  $R_2$  (in ohms) are:

- A 3, 4
- B 2, 12
- C 3, 16
- D 4, 12
- E 4, 16

Answer: D

### Question 4

Two wires made of the same material have the same lengths but different diameters. They are connected in parallel to a battery. The quantity that is NOT the same for the wires is:

- A the end-to-end potential difference
- B the current
- C the current density
- D the electric field
- E the electron drift velocity

### Question 4

Two wires made of the same material have the same lengths but different diameters. They are connected in parallel to a battery. The quantity that is NOT the same for the wires is:

- A the end-to-end potential difference
- B the current
- C the current density
- D the electric field
- E the electron drift velocity

Answer: B

### Question 5

Resistor 1 has twice the resistance of resistor 2. They are connected in parallel to a battery. The ratio of the thermal energy generation rate in resistor 1 to that in resistor 2 is:

- A 1 : 4
- B 1 : 2
- C 1 : 1
- D 2 : 1
- E 4 : 1



### Question 5

Resistor 1 has twice the resistance of resistor 2. They are connected in parallel to a battery. The ratio of the thermal energy generation rate in resistor 1 to that in resistor 2 is:

- A 1 : 4
- B 1 : 2
- C 1 : 1
- D 2 : 1
- E 4 : 1

Answer: B

### Question 6

A series circuit consists of a battery with internal resistance  $r$  and an external resistor  $R$ . If these two resistances are equal ( $r = R$ ) then the thermal energy generated per unit time by the internal resistance  $r$  is:

- A the same as by  $R$
- B half that by  $R$
- C twice that by  $R$
- D one-third that by  $R$
- E unknown unless the emf is given

### Question 6

A series circuit consists of a battery with internal resistance  $r$  and an external resistor  $R$ . If these two resistances are equal ( $r = R$ ) then the thermal energy generated per unit time by the internal resistance  $r$  is:

- A the same as by  $R$
- B half that by  $R$
- C twice that by  $R$
- D one-third that by  $R$
- E unknown unless the emf is given

Answer: A

### Question 7

In the capacitor discharge formula  $q = q_0 e^{-\frac{t}{RC}}$  the symbol  $t$  represents:

- A the time constant
- B the time it takes for C to lose the fraction  $\frac{1}{e}$  of its initial charge
- C the time it takes for C to lose the fraction  $(1 - \frac{1}{e})$  of its initial charge
- D the time it takes for C to lose essentially all of its initial charge
- E none of the above

### Question 7

In the capacitor discharge formula  $q = q_0 e^{-\frac{t}{RC}}$  the symbol  $t$  represents:

- A the time constant
- B the time it takes for C to lose the fraction  $\frac{1}{e}$  of its initial charge
- C the time it takes for C to lose the fraction  $(1 - \frac{1}{e})$  of its initial charge
- D the time it takes for C to lose essentially all of its initial charge
- E none of the above

Answer: E