

$$C_1 = 6 \mu\text{F}$$

$$C_2 = 4 \mu\text{F}$$

$$C_3 = 7 \mu\text{F}$$

$$C_4 = 4 \mu\text{F}$$

$$C_5 = 2 \mu\text{F}$$

$$V = 12 \text{ V}$$


A

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{6} + \frac{1}{4} = 2 \mu\text{F}$$

$$C_{123} = C_{12} + C_3 = 9.4$$

$$\frac{1}{C_{45}} = \frac{1}{C_{123}} + \frac{1}{C_4} + \frac{1}{C_5} = \boxed{1.17 \mu\text{F}}$$

B)

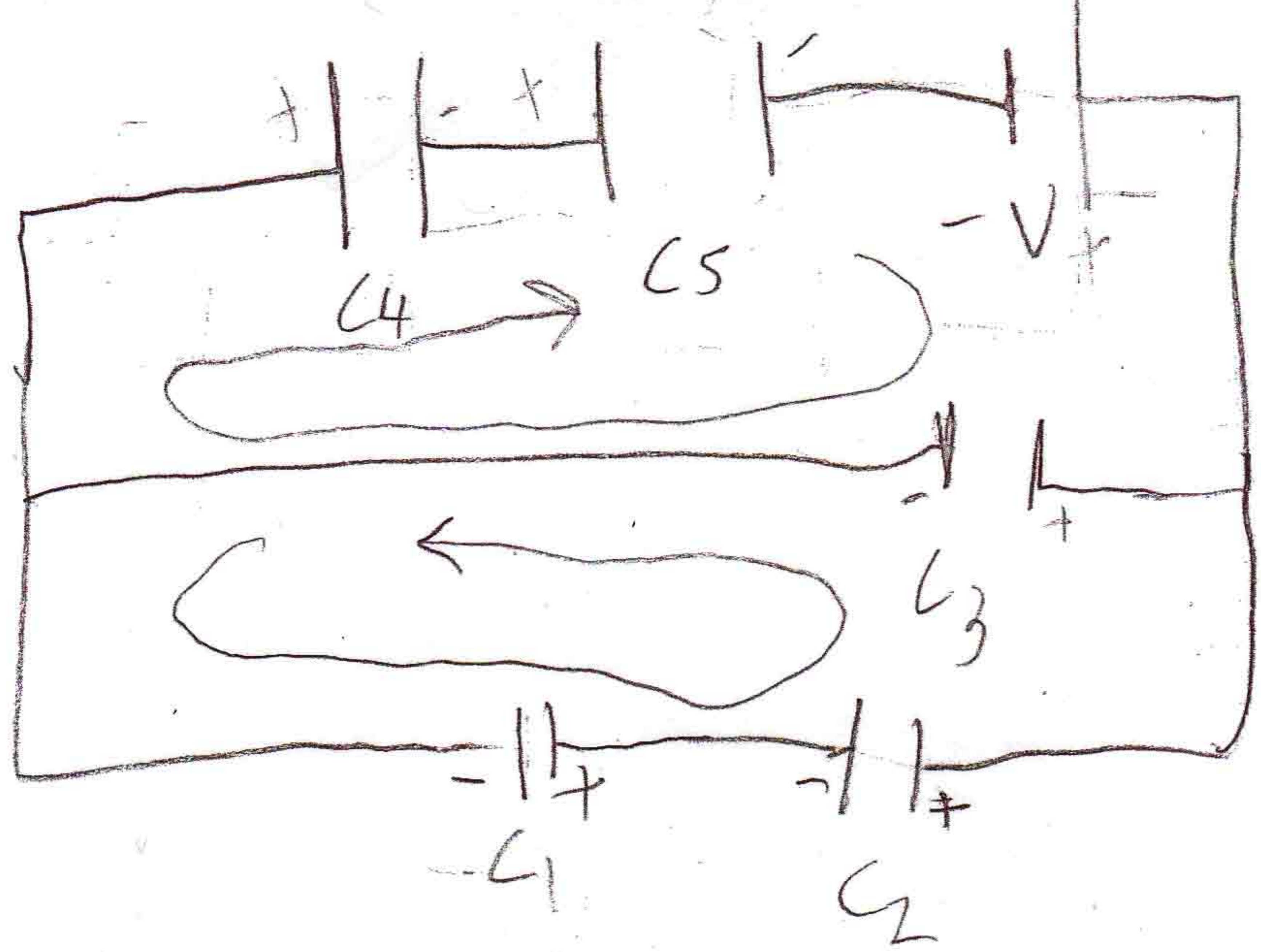

- $q_1 = 3.75 \mu\text{C}$      $V_1 = .625 \text{V}$
- $q_2 = 3.75 \mu\text{C}$      $V_2 = .845 \text{V}$
- $q_3 = 10.29 \mu\text{C}$      $V_3 = 1.47 \text{V}$
- $q_4 = 14.04 \mu\text{C}$      $V_4 = 3.51 \text{V}$
- $q_5 = 14.04 \mu\text{C}$      $V_5 = 7.02 \text{V}$
- $q_t = 14.04 \mu\text{C}$      $V_t = 12 \text{V}$

$Q = Q_2 + Q_3$

$Q_2 = Q_1$

$Q_1 + Q_3 = Q_4$

$Q_4 = Q_5$

$Q_5 = Q$

$Q = (12)(1.17 \mu\text{F})$

$Q = 14.04 \mu\text{C} = Q_4 = Q_5$

$V_4 = \frac{14.04 \mu\text{C}}{4 \mu\text{F}} = 3.51 \text{V}$

$V_5 = \frac{14.04 \mu\text{C}}{2 \mu\text{F}} = 7.02 \text{V}$

$V - V_3 - V_4 - V_5 = 0$   
 $12 = V_3 + 3.51 + 7.02$

$V_3 = 1.47 \text{V}$

$q_3 = (1.47)(7 \mu\text{F}) = 10.29$

$V - V_3 - V_4 - V_5 = 0$

$V_1 + V_2 - V_3 = 0$

$Q_1 = V_1 C_1$

$Q_2 = V_2 C_2$

$Q_3 = V_3 C_3$

$Q_4 = V_4 C_4$

$Q_5 = V_5 C_5$

$Q = VC$

$Q_2 = Q_1 = Q - Q_3$

$Q_2 = Q_1 = 3.75 \mu\text{C}$

$V_1 = \frac{3.75 \mu\text{C}}{6 \mu\text{F}} = .625$

$V_1 + V_2 - V_3 = 0$

$V_2 = V_3 - V_1$

$V_2 = .845$

$$c) V_{ab} = V_2 = .845V$$

d) Total energy if separation in  $d_5 = 10 \times 10^{-6} m$   
Find the electric field

$$U_{\text{tot}} = \frac{1}{2} C_{\text{eq}} V^2 = \frac{1}{2} (1.17 \mu F) (12)^2 = \boxed{84.24 \mu F}$$

$$E_5 = \frac{V_5}{d_5} = \frac{7.02}{10 \times 10^{-6}} = 702000$$