



$$E_1 = 8 \quad R_1 = 4$$

$$E_2 = 10 \quad R_2 = 6$$

$$E_3 = 12 \quad R_3 = 2$$

$$R_4 = 8$$

$$A) I_1 = I_2 + I_3$$

$$E_1 - I_2 R_2 + E_2 - I_1 R_1 = 0 \Rightarrow I_1 = 4.5 - 1.5 I_2$$

$$8 - 6I_2 + 10 - 4I_1 = 0$$

$$I_1 = 4.5 - 1.5(2.16)$$

$$I_1 = 1.26 A$$

$$-E_3 - E_2 + I_2 R_2 - I_3 R_3 - I_3 R_4 = 0 \Rightarrow I_3 = -2.2 + 0.6 I_2$$

$$-12 - 10 + 6I_2 - 2I_3 - 8I_3 = 0$$

$$I_3 = -2.2 + 0.6(2.16)$$

$$I_3 = -0.904 A$$

$$-22 + 6I_2 = 10I_3$$

$$4.5 - 1.5I_2 = I_2 - 2.2 + 0.6I_2$$

$$6.7 = 3.1I_2$$

$$2.16 A = I_2$$

$I_1 = 1.26 A$	correct
$I_2 = 2.16 A$	correct
$I_3 = -0.904$	incorrect

$$B) P_{R_1} = I_1^2 R_1 = (1.26)^2 (4) = 6.35 \text{ W}$$

$$P_{R_2} = I_2^2 R_2 = (2.16)^2 (6) = 27.99 \text{ W}$$

$$P_{R_3} = I_3^2 R_3 = (.904)^2 (2) = 1.63 \text{ W}$$

$$P_{R_4} = I_3^2 R_4 = (.904)^2 (8) = 6.54 \text{ W}$$

$$C) P_{\epsilon_1} = I_1 \epsilon_1 = (1.26)(8) = 10.08 \text{ W Del. by}$$

$$P_{\epsilon_2} = I_2 \epsilon_2 = (2.16)(10) = 21.6 \text{ W Del. by}$$

$$P_{\epsilon_3} = I_3 \epsilon_3 = (.904)(12) = 10.85 \text{ W Del. By}$$

$$D) |\Delta V| = |I_2 R_2 + \epsilon_2|$$

$$\Delta V = 2.96 \text{ V}$$